

Circuit Design with VHDL **1st Edition**

Volnei A. Pedroni, MIT Press, 2004

Selected Exercise Solutions

Problem 2.1: Multiplexer

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY mux IS  
    PORT (  
        a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);  
        sel: IN STD_LOGIC_VECTOR(1 DOWNTO 0);  
        c: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));  
END mux;  
-----  
ARCHITECTURE example OF mux IS  
BEGIN  
    PROCESS (a, b, sel)  
    BEGIN  
        IF (sel="00") THEN  
            c <= "00000000";  
        ELSIF (sel="01") THEN  
            c <= a;  
        ELSIF (sel="10") THEN  
            c <= b;  
        ELSE  
            c <= (OTHERS => 'Z'); --or c<="ZZZZZZZZ";  
        END IF;  
    END PROCESS;  
END example;  
-----
```

Problem 3.2: Dealing with data types

First, recall figure 3.1, which shows four types of data structures. From it, we conclude the following:

a: a scalar of type BIT

b: a scalar of type STD_LOGIC

x: a 1D array (a vector) of type ARRAY1, whose 8 individual elements are of type STD_LOGIC

y: a 2D array (a matrix) of type ARRAY2, whose 4x8=32 individual elements are of type STD_LOGIC

w: a 1Dx1D array (another matrix) of type ARRAY3, whose 4 individual 8-element vectors are of type ARRAY1

z: another 1D array (another vector) whose 8 individual elements are again of type STD_LOGIC

Therefore:

```
a <= x(2);
```

a: scalar, type BIT

x(2): scalar, type STD_LOGIC

Assignment is illegal (type mismatch)

```
b <= x(2);
```

b: scalar, type STD_LOGIC

x(2): scalar, type STD_LOGIC

Assignment is legal

```
b <= y(3,5);
```

b: scalar, type STD_LOGIC

y(3,5): scalar, type STD_LOGIC, with valid indexing

Assignment is legal

```
b <= w(5)(3);
```

b: scalar, type STD_LOGIC

w(5)(3): scalar, type STD_LOGIC, but "5" is out of bounds

Assignment is illegal

```
y(1)(0) <= z(7);
```

y(1)(0): scalar, type STD_LOGIC, but indexing is incorrect because *y* is 2D (it should be *y*(1,0))

z(7): scalar, type STD_LOGIC

Assignment is illegal

```
x(0) <= y(0,0);
```

x(0): scalar, type STD_LOGIC

y(0,0): scalar, type STD_LOGIC, valid indexing

Assignment is legal

```
x <= "11110000";
```

x: 8-bit vector (1D)

Assignment would be legal if it contained 8 values instead of 7

```
a <= "00000000";
```

a: scalar, so can only have one bit

Assignment is illegal

```
y(1) <= x;
```

y(1): in principle, an 8-element vector, extracted from a 2D matrix, whose individual elements are of type STD_LOGIC; however, the indexing (slicing) of *y* is not valid, because the matrix is 2D, not 1Dx1D

x: an 8-element vector of type ARRAY1

Assignment is illegal (invalid slicing + type mismatch)

```
w(0) <= y;
```

w(0): row 0 of a 1Dx1D matrix, which is an 8-element vector of type ARRAY1

y: a 4x8 (2D) matrix

Assignment is illegal (size + type mismatches)

```
w(1) <= (7=>'1', OTHERS=>'0');
```

w(1): row 1 of a 1Dx1D matrix

Assignment is legal (*w*(1)<="10000000")

```
y(1) <= (0=>'0', OTHERS=>'1');
```

y(1): in principle, row 1 of a matrix, but the indexing is invalid, because the matrix is 2D, not 1Dx1D

Assignment *y*(1)<="11111110" is illegal

```
w(2)(7 DOWNT0 0) <= x;
```

w(2)(7 DOWNT0 0): row 2 of a 1Dx1D matrix, which is an 8-element vector of type ARRAY1

x: an 8-element vector of type ARRAY1

Assignment is legal

Note: w(2) <= x would be fine too

```
w(0)(7 DOWNT0 6) <= z(5 DOWNT0 4);
```

w(0)(7 DOWNT0 6): the leftmost 2 elements of row 0 of a 1Dx1D matrix, being each row an 8-element vector of type ARRAY1

z(5 DOWNT0 4): 2 elements of an 8-element STD_LOGIC_VECTOR

Assignment is illegal (type mismatch)

```
x(3) <= x(5 DOWNT0 5);
```

x(3): a scalar of type STD_LOGIC

x(5 DOWNT0 5): also a scalar of type STD_LOGIC

Assignment is legal

```
b <= x(5 DOWNT0 5)
```

b: a scalar of type STD_LOGIC

x(5 DOWNT0 5): also a scalar of type STD_LOGIC

Assignment is legal

```
y <= ((OTHERS=>'0'), (OTHERS=>'0'), (OTHERS=>'0'), "10000001");
```

y is a 2D matrix

Assignment is legal.

Note: Since y is 2D, some older compilers might not accept the vector-like assignments above, thus requiring the assignment to be made element by element (with GENERATE, for example).

Note: The assignment below is also legal.

```
y <= (( '0','0','0','0','0','0','0','0'),
      ('0','0','0','0','0','0','0','0'),
      ('0','0','0','0','0','0','0','0'),
      ('1','0','0','0','0','0','0','1'));
```

```
z(6) <= x(5);
```

z(6): scalar of type STD_LOGIC

x(5): also a scalar of type STD_LOGIC (though as a vector x is of type ARRAY1, as a scalar ("base" type) it is STD_LOGIC)

```
z(6 DOWNT0 4) <= x(5 DOWNT0 3);
```

z(6 DOWNT0 4): 3-element vector of type STD_LOGIC_VECTOR

x(5 DOWNT0 3): 3-element vector of type ARRAY1

Assignment is illegal (type mismatch)

```
z(6 DOWNT0 4) <= y(5 DOWNT0 3);
```

The indexing of y is invalid (slicing 2D array is generally not allowed)

Assignment is illegal

```
y(6 DOWNT0 4) <= x(3 TO 5);
```

The indexing of y is invalid (slicing 2D array is generally not allowed)

Indexing of x is in the wrong direction

Assignment is illegal

```
y(0, 7 DOWNT0 0) <= z;
```

y(0, 7 DOWNT0 0): in principle, row 0 of a matrix, but slicing 2D arrays is generally not supported

Assignment is illegal

```
w(2,2) <= '1';
```

w is 1Dx1D, so indexing should be w(2)(2)

Assignment is illegal

Problem 4.1: Operators

```

x1 <= a & c;           --x1 = "10010"
x2 <= c & b;           --x2 = "00101100"
x3 <= b XOR c;         --x3 = "1110"
x4 <= a NOR b(3);      --x4 = '0'
x5 <= b sll 2;         --x5 = "0000"
x6 <= b sla 2;         --x6 = "0000"
x7 <= b rol 2;         --x7 = "0011";
x8 <= a AND NOT b(0) AND NOT c(1); --x8 = '0'
d <= (5=>'0', OTHERS=>'1'); --d = "11011111"

```

Problem 5.1: Generic Multiplexer

Solution 1: In this solution, no package is employed. Notice however that x was not defined as a 1Dx1D or 2D structure (chapter 3); instead, it was specified as simply a long vector of length $m(2^n)$. Though this will not affect the result, such a “linearization” might be confusing sometimes, so is not recommended in general.

```

-----
ENTITY generic_mux IS
  GENERIC (
    n: INTEGER := 4; --number of selection bits
    m: INTEGER := 8); --number of bits per input
  PORT (
    x: IN BIT_VECTOR (m*2**n-1 DOWNT0 0);
    sel: IN INTEGER RANGE 0 TO 2**n-1;
    y: OUT BIT_VECTOR (m-1 DOWNT0 0));
END generic_mux;
-----
ARCHITECTURE generic_mux OF generic_mux IS
BEGIN
  gen: FOR i IN m-1 DOWNT0 0 GENERATE
    y(i) <= x(m*sel+i);
  END GENERATE gen;
END generic_mux;
-----

```

Solution 2: Here, a user-defined (in a package) type is employed

```

--- Package: -----
PACKAGE my_data_types IS
  TYPE matrix IS ARRAY (NATURAL RANGE <>, NATURAL RANGE <>) OF BIT;
END PACKAGE my_data_types;
-----

--- Main code: -----
USE work.my_data_types.all;
-----
ENTITY generic_mux IS
  GENERIC (
    inputs: INTEGER := 16; --number of inputs
    size: INTEGER := 8); --size of each input
  PORT (
    x: IN MATRIX (0 TO inputs-1, size-1 DOWNT0 0);
    sel: IN INTEGER RANGE 0 TO inputs-1;
    y: OUT BIT_VECTOR (size-1 DOWNT0 0));
END generic_mux;
-----
ARCHITECTURE arch OF generic_mux IS
BEGIN
  gen: FOR i IN size-1 DOWNT0 0 GENERATE
    y(i) <= x(sel, i);
  END GENERATE gen;
END arch;
-----

```

Problem 5.4: Unsigned adder

A possible solution is shown below (but see the NOTE that follows). The ports were considered to be of type STD_LOGIC (industry standard). Simulation results are included after the code.


```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all; --allows arith. operations w/ STD_LOGIC
-----
ENTITY adder IS
    PORT (
        a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        sum: OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
        cout: OUT STD_LOGIC);
END adder;
-----
ARCHITECTURE adder OF adder IS
    SIGNAL long_a, long_b, long_sum: STD_LOGIC_VECTOR(8 DOWNTO 0);
BEGIN
    long_a <= '0' & a;
    long_b <= '0' & b;
    long_sum <= long_a + long_b;
    sum <= long_sum(7 DOWNTO 0);
    cout <= long_sum(8);
END adder;
-----

```

NOTE: Even though the solution above is fine in principle, the recommended approach for arithmetic circuits is to explicitly convert the inputs to UNSIGNED or SIGNED (so it will be clear that the unsigned/signed issue was considered), do the computations, then return the result to STD_LOGIC_VECTOR (to be sent out).

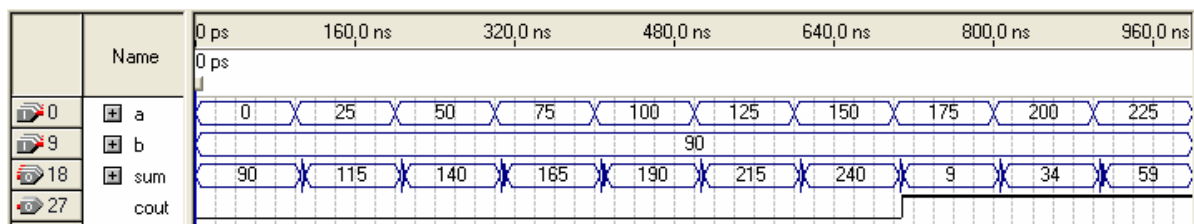The reader is invited to redo this problem taking into account the recommendation above.



Simulation results for Problem 5.4.

Problem 5.6: Binary-to-Gray code converter

The gray codeword $g(N-1:0)$ corresponding to a regular binary codeword $b(N-1:0)$ can be obtained as follows:

For $i = N-1$: $g(i) = b(i)$


For $i = N-2 \dots 0$: $g(i) = b(i) \oplus b(i+1)$

A corresponding *generic* VHDL code is presented below, followed by simulation results for $N=4$.

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----
ENTITY gray_encoder IS
    GENERIC (N: INTEGER := 4);
    PORT (b: IN STD_LOGIC_VECTOR(N-1 DOWNTO 0);
          g: OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0));
END gray_encoder;
-----
ARCHITECTURE gray_encoder OF gray_encoder IS
BEGIN
    g(N-1) <= b(N-1);
    g(N-2 DOWNTO 0) <= b(N-2 DOWNTO 0) XOR b(N-1 DOWNTO 1);
END gray_encoder;

```

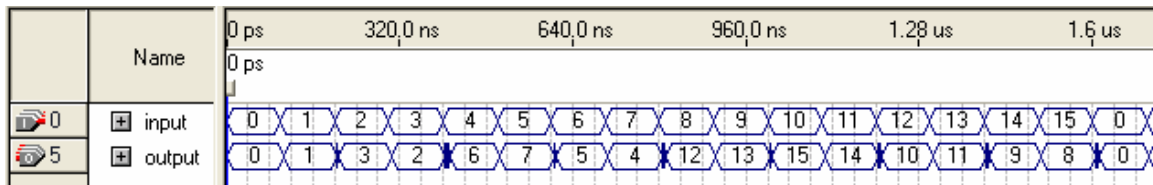

Simulation results for Problem 5.6.

Problem 6.2: Four-stage shift register

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----
ENTITY shift_reg IS
    PORT (
        clk, din: IN STD_LOGIC;
        dout: OUT STD_LOGIC);
END shift_reg;
-----
ARCHITECTURE shift_reg OF shift_reg IS
    SIGNAL d: STD_LOGIC_VECTOR(3 DOWNTO 0);
BEGIN
    PROCESS(clk)
    BEGIN
        IF (clk'EVENT AND clk='1') THEN
            d <= din & d(3 DOWNTO 1);
        END IF;
    END PROCESS;
    dout <= d(0);
END shift_reg;
-----

```


Problem 6.4: Generic frequency divider

```

----Clock frequency is divided by N-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----
ENTITY clock_divider IS
    GENERIC (N: POSITIVE := 7);
    PORT (clkkin: IN STD_LOGIC;
          clkout: OUT STD_LOGIC);
END ENTITY;
-----
ARCHITECTURE clock_divider OF clock_divider IS
BEGIN
    PROCESS (clkkin)
        VARIABLE count: INTEGER RANGE 0 TO N;
    BEGIN
        IF (clkkin'EVENT AND clkkin='1') THEN
            count := count + 1;
            IF (count=N/2) THEN
                clkout <= '1';
            ELSIF (count=N) THEN
                clkout <= '0';
                count := 0;
            END IF;
        END IF;
    END PROCESS;
END ARCHITECTURE;
-----

```

NOTE: In the solution above the duty cycle is not symmetric when N is odd (see simulation results below). Can you rewrite this code such that the duty cycle is always 50% (for both even and odd values of N)?

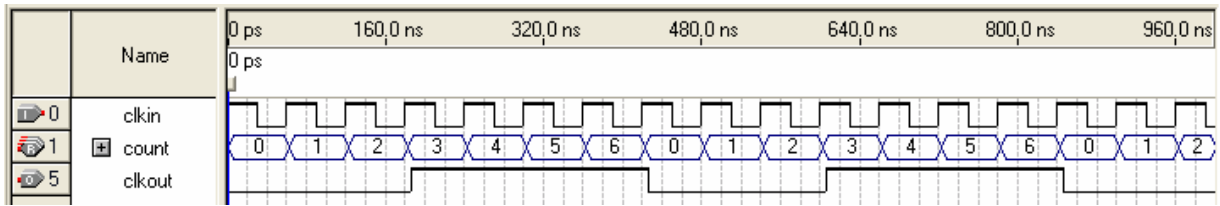Simulation results for $N=7$ in Problem 6.4.**Problem 6.12: Vector shifter**

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----
ENTITY vector_shifter IS
    GENERIC (n: INTEGER := 7); -- number of bits at input
    PORT (
        input: IN STD_LOGIC_VECTOR (n-1 DOWNTO 0);
        sel: IN INTEGER RANGE 0 TO n;
        output: OUT STD_LOGIC_VECTOR(2*n-1 DOWNTO 0));
END vector_shifter;
-----
ARCHITECTURE behavior OF vector_shifter IS
BEGIN
    PROCESS (input, sel)
        VARIABLE temp: STD_LOGIC_VECTOR(output'LEFT DOWNTO 0);
    BEGIN
        temp := (OTHERS => '0');
        FOR i IN input'RANGE LOOP
            temp(sel+i) := input(i);
        END LOOP;
        output <= temp;
    END PROCESS;
END behavior;
-----

```

Problem 6.17: DFF

Architecture 1: A truly D-type flip-flop with asynchronous reset (same as in Example 6.1) .

Architecture 2: Only the clock appears in the sensitivity list, causing the reset to be *synchronous*.

Architecture 3: `clk'EVENT` is not associated with a test (AND `clk='1'`, for example). Such test is mandatory in most compilers, so this is not a correct code.

Architecture 4: Here the contents of sections 6.10 and 7.5 are helpful. Notice that no signal assignment is made at the transition of another signal, signifying that, in principle, no flip-flop is wanted (thus a combinational circuit). However, only one of the input signals appears in the sensitivity list, and an incomplete truth table for q is specified in the code, causing the inference of a latch to hold the value of q (a “pseudo” combinational circuit).

Architecture 5: The situation here is even more awkward than that above. Besides inferring again a latch, changes of d also cause the process to be run. The resulting circuit is very unlikely to be of any interest.

Problem 7.1: Legal/illegal assignments

Suggestion: Before solving this problem, review the solution of Problem 3.2.

```

x <= 5;                --legal
x <= y(5);             --illegal (type mismatch)
z <= '1';              --illegal (should be "!=" for variable)
z := y(5);             --legal

```

```

WHILE i IN 0 TO max LOOP...      --legal (both bounds are static)
FOR i IN 0 TO x LOOP...          --illegal (bounds must be static)
G1: FOR i IN 0 TO max GENERATE... --legal (both bounds are static)
G1: FOR i IN 0 TO x GENERATE...   --illegal (bounds must be static)

```


Problem 7.6: Generic address decoder

In the solution below, all ports are of type STD_LOGIC (industry standard). Simulation results (for $N=3$) are included after the code. Regarding the glitches in the simulation results, recall that they are normal in combinational circuits when a signal depends on multiple bits, because the values of such bits do not change all at exactly the same time.

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
-----
ENTITY address_decoder IS
    GENERIC (N: POSITIVE := 3); --# of input bits
    PORT (ena: IN STD_LOGIC;
          address: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
          wordline: OUT STD_LOGIC_VECTOR(2**N-1 DOWNT0 0));
END ENTITY;
-----
ARCHITECTURE address_decoder OF address_decoder IS
BEGIN
    PROCESS (ena, address)
        VARIABLE internal: STD_LOGIC_VECTOR(2**N-1 DOWNT0 0);
        VARIABLE addr: NATURAL RANGE 0 TO 2**N-1;
    BEGIN
        addr := CONV_INTEGER(address);
        internal := (OTHERS => '1');
        IF (ena='1') THEN
            internal(addr) := '0';
        END IF;
        wordline <= internal;
    END PROCESS;
END ARCHITECTURE;
-----

```

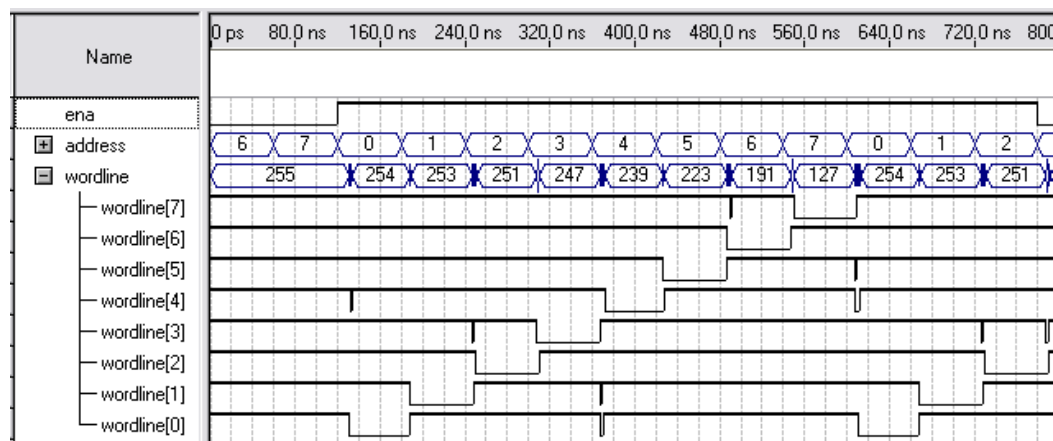

Simulation results for Problem 7.6.

Problem 8.1: Finite State Machine

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----
ENTITY fsm IS
    PORT (
        inp, clk, rst: IN STD_LOGIC;
        outp: OUT STD_LOGIC_VECTOR (1 DOWNT0 0));
END fsm;

```




```

-----
ARCHITECTURE fsm OF fsm IS
  TYPE state IS (statel, state2, state3, state4);
  SIGNAL pr_state, nx_state: state;
BEGIN
  ----- Lower section: -----
  PROCESS (rst, clk)
  BEGIN
    IF (rst='1') THEN
      pr_state <= statel;
    ELSIF (clk'EVENT AND clk='1') THEN
      pr_state <= nx_state;
    END IF;
  END PROCESS;
  ----- Upper section: -----
  PROCESS (inp, pr_state)
  BEGIN
    CASE pr_state IS
      WHEN statel =>
        outp <= "00";
        IF (inp='1') THEN
          nx_state <= state2;
        ELSE
          nx_state <= statel;
        END IF;
      WHEN state2 =>
        outp <= "01";
        IF (inp='1') THEN
          nx_state <= state4;
        ELSE
          nx_state <= state3;
        END IF;
      WHEN state3 =>
        outp <= "10";
        IF (inp='1') THEN
          nx_state <= state4;
        ELSE
          nx_state <= state3;
        END IF;
      WHEN state4 =>
        outp <= "11";
        IF (inp='1') THEN
          nx_state <= statel;
        ELSE
          nx_state <= state2;
        END IF;
    END CASE;
  END PROCESS;
END fsm;
-----

```

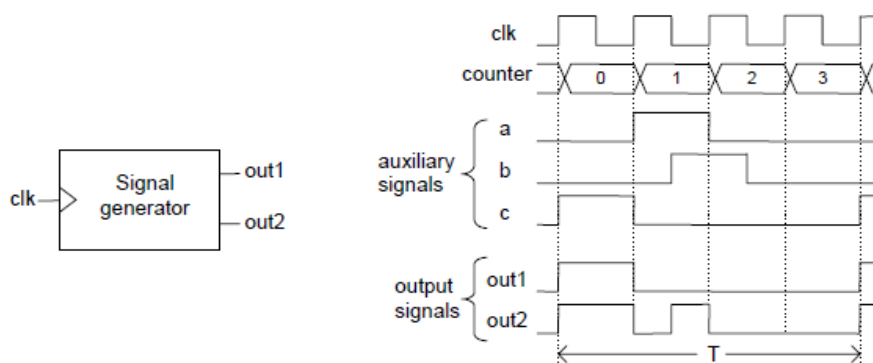Problem 8.6: Signal generator without the FSM approach

Physical circuits, design, and operation of sequential circuits are described in chapter 14 of [1]. The solution that follows is based on the theory presented there. The corresponding signals are depicted in the figure below.




Signals employed in the solution of Problem 8.6.

In this case (figure above), three auxiliary signals (*a*, *b*, *c*) are created, from which *out1* and *out2* are then derived using conventional gates. As described in chapter 14 of [1], the fundamental point here is to guarantee that the outputs are not prone to glitches. To guarantee glitch-free outputs, all three auxiliary signals are registered (i.e., stored in DFFs); consequently, given that no two signals that affect the gates' outputs change at the same clock edge, glitch-free outputs are automatically generated. A corresponding VHDL follows, along with simulation results.

```

-----
ENTITY signal_generator IS
    PORT (clk: IN BIT;
          out1, out2: OUT BIT);
END ENTITY;
-----
ARCHITECTURE signal_generator OF signal_generator IS
    SIGNAL a, b, c: BIT;
    SIGNAL counter: INTEGER RANGE 0 TO 3;
BEGIN
    ----Creating a counter:-----
    PROCESS (clk)
        VARIABLE count: INTEGER RANGE 0 TO 4;
    BEGIN
        IF (clk'EVENT AND clk='1') THEN
            count := count + 1;
            IF (count=4) THEN
                count := 0;
            END IF;
        END IF;
        counter <= count;
    END PROCESS;
    ----Generating signal a:-----
    PROCESS (clk)
    BEGIN
        IF (clk'EVENT AND clk='1') THEN
            IF (counter=0) THEN
                a <= '1';
            ELSE
                a <= '0';
            END IF;
        END IF;
    END PROCESS;
    ----Generating signal b:-----
    PROCESS (clk)
    BEGIN
        IF (clk'EVENT AND clk='0') THEN
            IF (counter=1) THEN
                b <= '1';
            ELSE
                b <= '0';
            END IF;
        END IF;
    END PROCESS;
    ----Generating signal c:-----
    PROCESS (clk)
    BEGIN
        IF (clk'EVENT AND clk='1') THEN
            IF (counter=3) THEN
                c <= '1';
            ELSE
                c <= '0';
            END IF;
        END IF;
    END PROCESS;
    ----Generating the outputs:-----
    out1 <= c;
    out2 <= (a AND b) OR c;
END ARCHITECTURE;
-----

```

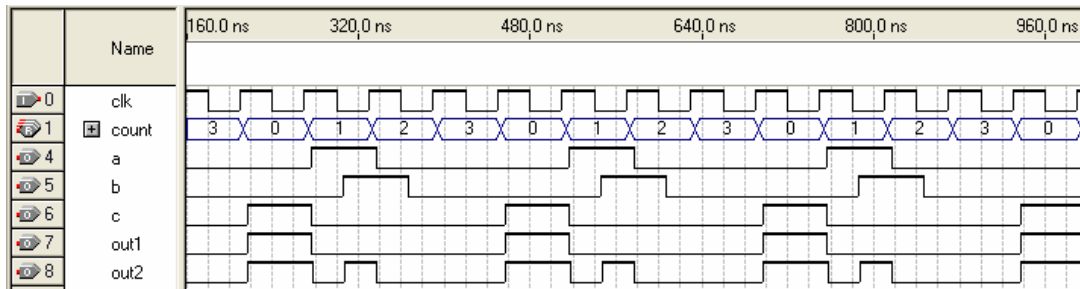

Simulation results for Problem 8.6.

Problem 10.2: Carry-ripple adder constructed with components

```

-----The component (full-adder unit):-----
ENTITY FAU IS
    PORT (a, b, cin: IN BIT;
          s, cout: OUT BIT);
END FAU;
-----

ARCHITECTURE full_adder OF FAU IS
BEGIN
    s <= a XOR b XOR cin;
    cout <= (a AND b) OR (a AND cin) OR (b AND cin);
END full_adder;
-----

-----Main code:-----
ENTITY carry_ripple_adder IS
    GENERIC (N : INTEGER := 8); --number of bits
    PORT (a, b: IN BIT_VECTOR(N-1 DOWNT0 0);
          cin: IN BIT;
          s: OUT BIT_VECTOR(N-1 DOWNT0 0);
          cout: OUT BIT);
END carry_ripple_adder;
-----

ARCHITECTURE structural OF carry_ripple_adder IS
    SIGNAL carry: BIT_VECTOR(N DOWNT0 0);
    COMPONENT FAU IS
        PORT (a, b, cin: IN BIT; s, cout: OUT BIT);
    END COMPONENT;
BEGIN
    carry(0) <= cin;
    generate_adder: FOR i IN a'RANGE GENERATE
        adder: FAU PORT MAP (a(i), b(i), carry(i), s(i), carry(i+1));
    END GENERATE;
    cout <= carry(N);
END structural;
-----

```

Problem 11.1: Conversion from INTEGER to STD_LOGIC_VECTOR

A VHDL code for this exercise is shown below. To test it, just a jumper from the input to the output was used, in which case the compiler must give equations of the type $output(i)=input(i)$, for $i=0, 1, \dots, N-1$. A similar function can be found in the standard package *std_logic_arith*, available in the library of your VHDL synthesis software. Note that in the solution below the function was located in the main code; to install it in a package, just follow the instruction in chapter 11 (see example 11.4, for example).

```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----

ENTITY data_converter IS
    GENERIC (N: NATURAL := 4); --number of bits
    PORT (input: IN INTEGER RANGE 0 TO 2**N-1;
          output: OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0));
END data_converter;

```


```

-----
ARCHITECTURE data_converter OF data_converter IS
  SIGNAL x: STD_LOGIC_VECTOR(N-1 DOWNT0 0);
  -----
  FUNCTION conv_std_logic(arg: INTEGER; size: POSITIVE)
  RETURN STD_LOGIC_VECTOR IS
    VARIABLE temp: INTEGER RANGE 0 TO 2**size-1;
    VARIABLE result: STD_LOGIC_VECTOR(size-1 DOWNT0 0);
  BEGIN
    temp := arg;
    FOR i IN result'RANGE LOOP
      IF (temp >= 2**i) THEN
        result(i) := '1';
        temp := temp - 2**i;
      ELSE
        result(i) := '0';
      END IF;
    END LOOP;
    RETURN result;
  END conv_std_logic;
  -----
BEGIN
  output <= conv_std_logic(input, N);
END data_converter;
-----

```

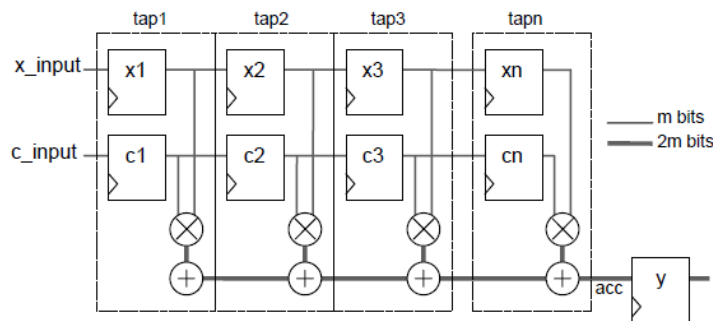Problem 12.4: General-purpose FIR filter

In this example, only integers are employed. A block diagram for the circuit is shown below. It contains two shift registers, which store the input values (x) and the filter coefficients (c). It contains also a register to store the accumulated (acc) value, producing the filter output (y). The total number of taps is n , with m bits used to represent x and c , and $2m$ bits for the after-multiplication paths. Hence a total of $2m(n+1)$ flip-flops are required. Observe that the taps are all alike, so COMPONENT can be used to easily implement this circuit. A slightly more difficult (non-structural) solution is shown below; the structural option (with COMPONENT) is left to the reader. Note that the code includes overflow check. Simulation results are also included.



```


-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all; --package needed for SIGNED
-----
ENTITY FIR IS
  GENERIC (n: INTEGER := 4; --number of coefficients
           m: INTEGER := 4); --number of bits per coefficient
  PORT (clk, rst: IN STD_LOGIC;
        load: STD_LOGIC; --to enter new coefficient values
        run: STD_LOGIC; --to compute the output
        x_input, coef_input: IN SIGNED(m-1 DOWNT0 0);
        y: OUT SIGNED(2*m-1 DOWNT0 0);
        overflow: OUT STD_LOGIC);
END FIR;
-----
ARCHITECTURE FIR OF FIR IS
  TYPE internal_array IS ARRAY (1 TO n) OF SIGNED(m-1 DOWNT0 0);
  SIGNAL c: internal_array; --stored coefficients
  SIGNAL x: internal_array; --stored input values
BEGIN

```

```

PROCESS (clk, rst)
  VARIABLE prod, acc: SIGNED(2*m-1 DOWNT0 0) := (OTHERS=>'0');
  VARIABLE sign_prod, sign_acc: STD_LOGIC;
BEGIN
  --Reset:-----
  IF (rst='1') THEN
    FOR i IN 1 TO n LOOP
      FOR j IN m-1 DOWNT0 0 LOOP
        x(i)(j) <= '0';
      END LOOP;
    END LOOP;
    --Shift registers:-----
  ELSIF (clk'EVENT AND clk='1') THEN
    IF (load='1') THEN
      c <= (coef_input & c(1 TO n-1));
    ELSIF (run='1') THEN
      x <= (x_input & x(1 TO n-1));
    END IF;
  END IF;
  --MACs and output (w/ overflow check):---
  acc := (OTHERS=>'0');
  FOR i IN 1 TO n LOOP
    prod := x(i)*c(i);
    sign_prod := prod(2*m-1);
    sign_acc := acc(2*m-1);
    acc := prod + acc;
    IF (sign_prod=sign_acc AND acc(2*m-1)/=sign_acc) THEN
      overflow <= '1';
    ELSE
      overflow <= '0';
    END IF;
  END LOOP;
  IF (clk'EVENT AND clk='1') THEN
    y <= acc;
  END IF;
END PROCESS;
END FIR;

```

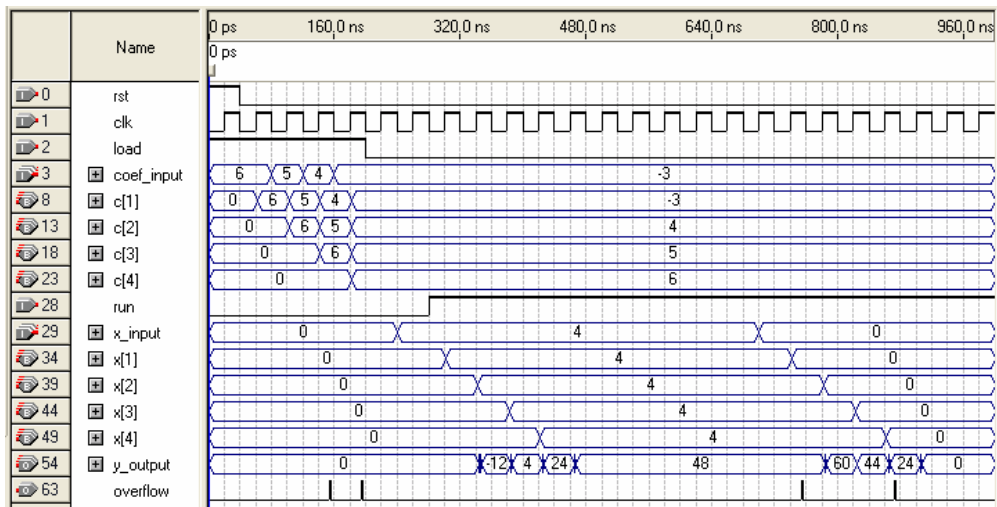

Simulation results for Problem 12.4.